

**ELECTRONIC DEVICES & CIRCUITS (19APCO403T)**

(Electronics &amp; Communication Engineering)

Time: 3 Hours

Max Marks: 70

**PART-A(Compulsory)**

(10\*2= 20 M)

Answer the following			UNIT	Marks
✓1	✓a)	Draw the V-I characteristics of UJT	I	2
	b)	What is the difference between DIAC and TRIAC	I	2
	✓c)	Draw the waveforms of output of full wave rectifier with & without filters	II	2
	✓d)	What is the difference between L-section & pi filters?	II	2
	✓e)	What is Bias Compensation?	III	2
	✓f)	What is the difference between CC and CE configurations?	III	2
	✓g)	What is the difference between Enhancement mode & Depletion mode?	IV	2
	✓h)	What is the difference between n-channel & p-channel JFET?	IV	2
	✓i)	Explain how JFET acts like a switch.	V	2
	✓j)	What are the different biasing circuits?	V	2

**PART-B**

(5\*10= 50 M)

**Answer One Full Question from each unit; All questions carry EQUAL marks.**

UNIT-I		
2	Explain the construction, Operation and Characteristics of Tunnel diode with the help of Energy band diagram.	10 M

(OR)

✓3	What is SCR? Explain its operation and V-I characteristics	10 M
----	--	------

**UNIT-II**

4	Explain in detail the operation of Clipping and Clamping circuits with waveforms	10 M
---	--	------

(OR)

✓5	Explain the construction, operation, and characteristics of Zener diode.	10 M
----	--	------

**UNIT-III**

✓6.	Compare and differentiate between the different configurations of BJT	10 M
-----	---	------

(OR)

7	Explain how BJT acts as a switch and Amplifier	10 M
---	--	------

**UNIT-IV**

8	Explain the construction, principle of operation & applications of JFET	10 M
---	---	------

(OR)

✓9.	Explain the construction, principle of operation & applications of MOSFET	10 M
-----	---	------

#### UNIT-V

✓10	Explain how FET acts a switch and Amplifier.	10 M
-----	--	------

(OR)

11.	Explain in detail the different biasing circuits used using MOSFET	10 M
-----	--	------