
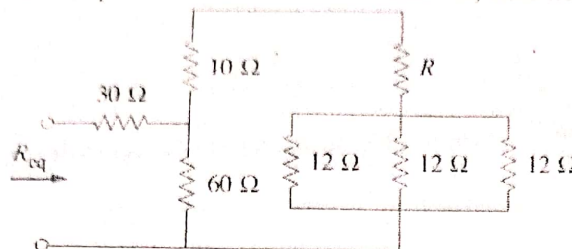
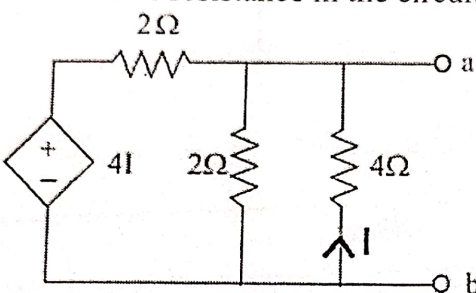


**PART-A**

(10\*2= 20 M)

Answer the following		UNIT	Marks
1	a) If $R_{eq} = 50 \Omega$ in the circuit shown, find R.	I	2
			
	b) Mention the properties of a tree w.r.t Network topology.	I	2
	c) What is Thevenin's resistance in the circuit shown?	II	2
			
	d) Three capacitors of 3 F each are connected in delta. Convert it into star connection.	II	2
	e) What is the value of $i(0^+)$ for the circuit shown?	III	2
			
	f) What is important role of initial conditions, in the transient analysis of RLC circuits?	III	2
	g) A primary coil has an inductance of $100\mu\text{H}$ which is connected in series with secondary coil having inductance of $240\mu\text{H}$ . Total inductance of this combination is measured as $150\mu\text{H}$ . Determine coefficient of coupling.	IV	2
	h) Prove that resonant frequency is geometric mean of half power frequencies.	IV	2
	i) Mention the condition of symmetry and reciprocity for Z parameters.	V	2
	j) Mention the classification of network functions	V	2

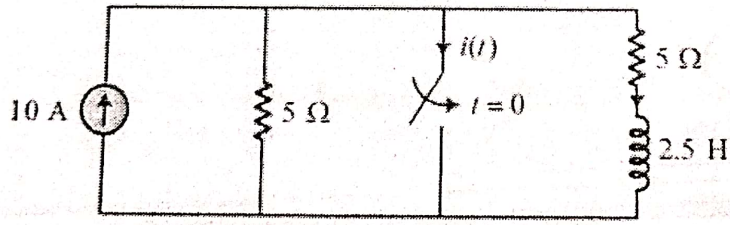

2	a)	Find Node voltages for the given circuit	5 M
	b)	Find cut-set schedule. Obtain equilibrium equations based on Node voltages.	5 M

(OR)



3	a)	Find $i_x$ and $v_x$ using Mesh analysis for the given circuit	5 M
	b)	Find tie-set schedule. Obtain equilibrium equations based on mesh equations.	5 M

### UNIT-II


4	a)	Find Thevenin's equivalent circuit between terminals a-b	5 M



(OR)

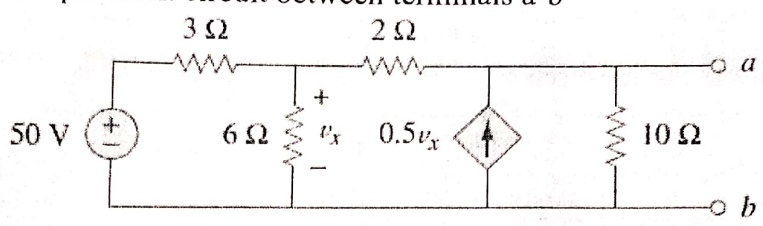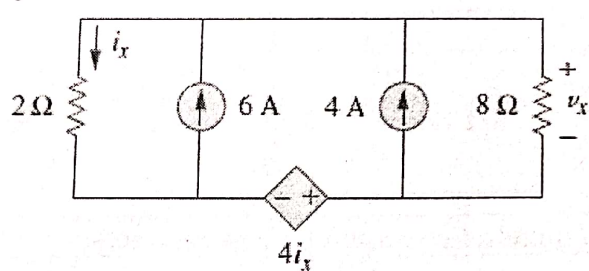5	a)	Find Norton's equivalent circuit between terminals a-b	5 M
			
	b)	Find $i_o$ using Superposition theorem.	5 M
			
UNIT-III			
6		Derive the expression for complete response of series RLC circuit for overdamped, critically damped, and underdamped cases.	10 M


(OR)

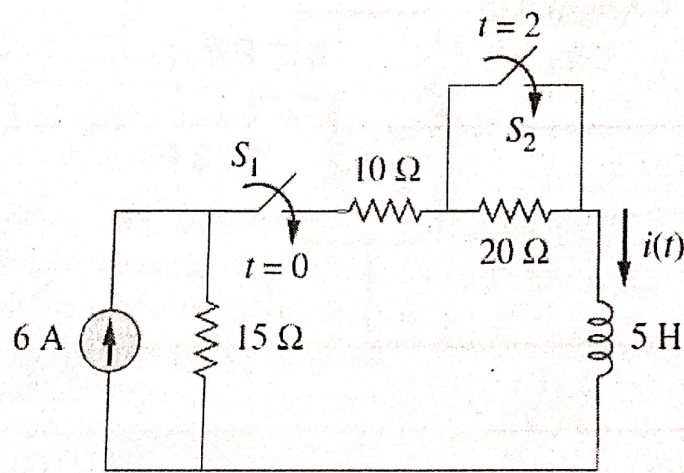7.	At $t=0$ , Switch-1 is closed, and Switch-2 is closed 2 secs later. Find $i(t)$ for $t>0$ . Calculate $i(1)$ and $i(3)$ .	10 M
		


UNIT-IV

8	a)	Find RMS value of the following equations (i) $V(t) = 2 + 3 \cos(100t) + 4 \cos(100t - 120^\circ)$ V (ii) $i(t) = 4 + 6 \cos(25t) + 5 \sin(30t)$ A (iii) $v(t) = 6 \cos(25t) + 5 \cos^2(25t)$ V	6 M
	b)	Derive the expression for Bandwidth in series resonant circuit	4 M

(OR)

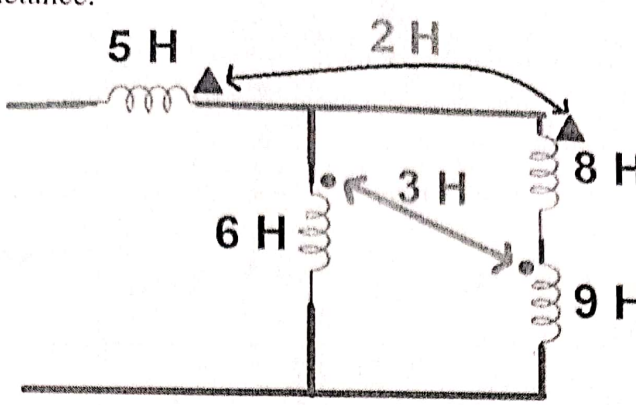9.	Obtain the electrical equivalent of the following magnetically coupled circuit. Also find its equivalent inductance.	10 M
		

### UNIT-V

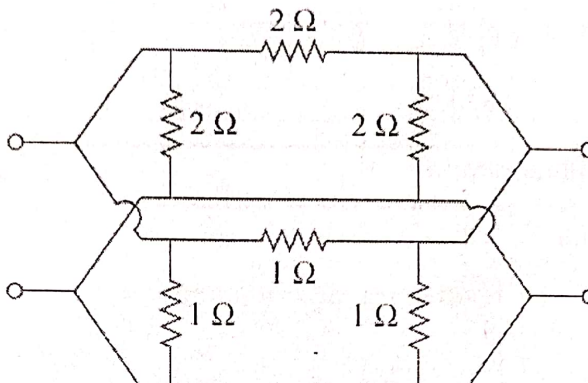10	a) Find h parameters for the given circuit	5 M
		
b)	Derive the reciprocal and symmetric condition for Z parameters.	5 M

(OR)

11.	Find the network functions $Z_{11}$ and $G_{12}$ for the circuit shown.	10 M
